

Indian Institute of Technology Kharagpur

AUTUMN Semester, 2018

COMPUTER SCIENCE AND ENGINEERING

Computer Organization Laboratory

Assignment-4: Verilog Design of Binary Adders

Full Marks: 20

Time allowed: 6 hours

INSTRUCTIONS: Make one submission per group in the form of a single zipped folder containing your Verilog source code files(s) and Verilog testbench, and a report (in .pdf format) of the hardware resource requirement and time required to complete 8-bit additions. Name your submitted zipped folder as `Assgn_4_Grp_<Group_no>.zip` and (e.g. `Assgn_4_Grp_25.zip`). Inside each submitted source and testbench files, there should be a clear header describing the assignment no., problem no., semester, group no., and names of group members. Liberally comment your code to improve its comprehensibility.

1. **[Ripple Carry Adder]** Design (using Verilog), simulate and implement on FPGA an 8-bit ripple carry adder. Your design should consist of a cascade of eight full adders. Write a testbench to simulate it, and use the provided “.ucf/.xdc” file to demonstrate its operation on the FPGA. Note its hardware requirement and critical path delay from the synthesis report. The interface of your design should be:

```
module ripple_carry_adder (input [11:0] a, input [11:0] b, input cy_in, output [11:0] sum,
                           output cy_out);
```

(4 marks)

2. **[Hybrid Adder]** Design (using Verilog), simulate and implement on FPGA an 8-bit hybrid adder. Your design should consist of a cascade of two 4-bit carry lookahead adders. Write a testbench to simulate it, and use the provided “.ucf/.xdc” file to demonstrate its operation on the FPGA. Note its hardware requirement and critical path delay from the synthesis report. The interface of your design should be:

```
module hybrid_adder (input [11:0] a, input [11:0] b, input cy_in, output [11:0] sum,
                    output cy_out);
```

(6 marks)

3. **[Bit-serial Adder]** Design (using Verilog), simulate and implement on FPGA a bit-serial adder. Write a testbench to simulate it, and use the provided “.ucf/.xdc” file to demonstrate its operation on the FPGA. Note its hardware requirement and critical path delay from the synthesis report. The input-side shift-registers used in the datapath of your bit-serial adder should have “parallel load” capabilities such that the 8-bit operands can be loaded in each of them in one clock cycle. Come up with a proper interface of your design, which includes all input control signals and a clock signal.
- (8 marks)

4. Finally, submit a small 1-page report (in .pdf format) comparing the speed of operation and hardware requirements of the above three designs.
- (2 marks)
